

 [david3891](#) / [Digital-electronics-1](#)

< > Code

! Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡 Security

🔑 main ▼

...

[Digital-electronics-1](#) / [Labs](#) / [03-vivado](#) / README.md

david3891 Update README.md

🕒 History

👤 1 contributor

Raw


Blame



111 lines (80 sloc) | 2.93 KB

Labs 03-vivado

1) Obrázky a tabulky se zapojeními

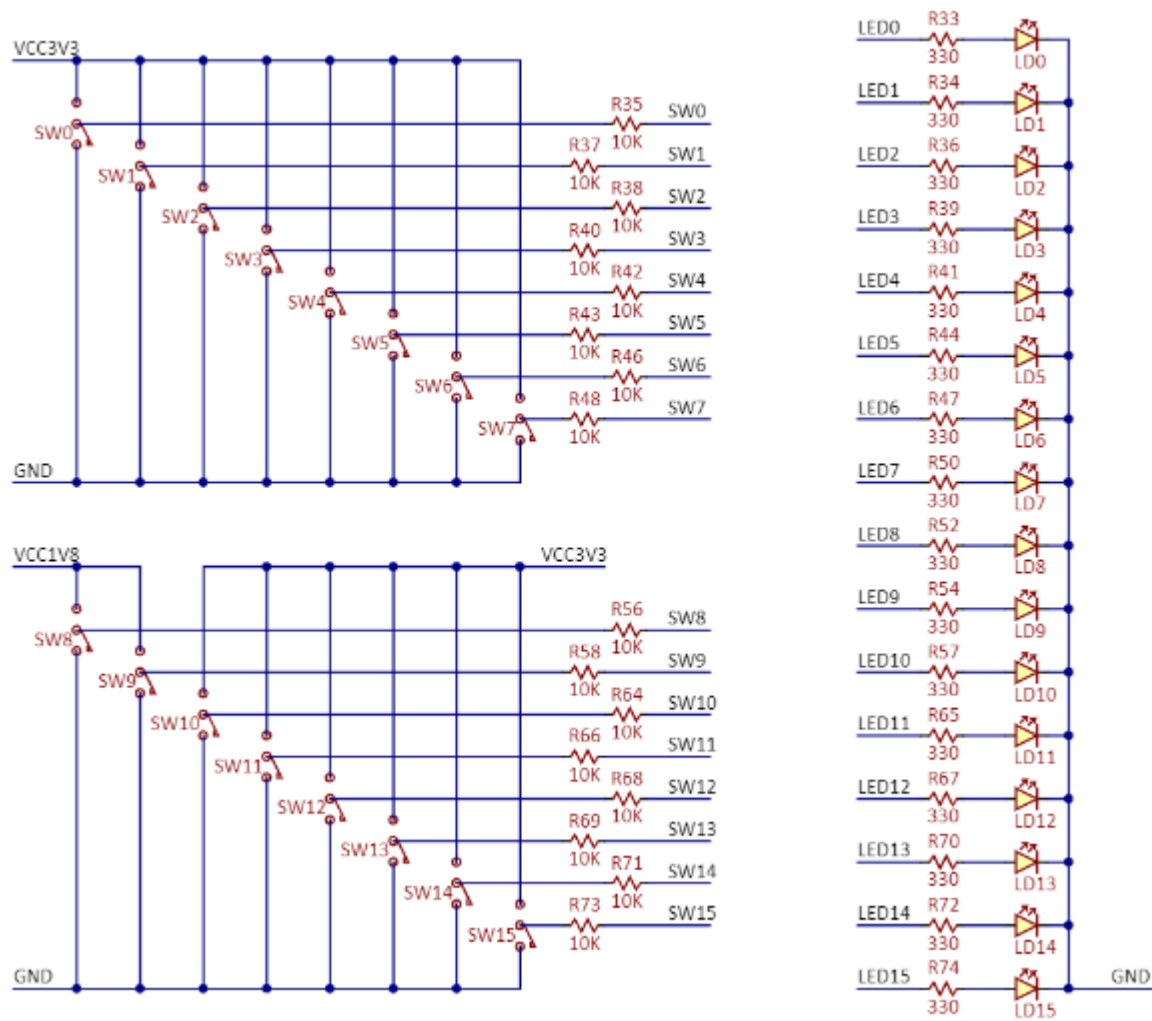

3/6

Switches	Resistors (10k Ω)	Connections
SW4	R42	R17
SW5	R43	T18
SW6	R46	U18
SW7	R48	R13
SW8	R56	T8
SW9	R58	U8
SW10	R64	R16
SW11	R66	T13
SW12	R68	H6
SW13	R69	U12
SW14	R71	U11
SW15	R73	V10

LEDs

Leds	Resistors (330 Ω)	Connections
LED0	R33	H17
LED1	R34	K15
LED2	R36	J13
LED3	R39	N14
LED4	R41	R18
LED5	R44	V17
LED6	R47	U17
LED7	R50	U16
LED8	R52	V16
LED9	R54	T15

Leds	Resistors (330Ω)	Connections
LED10	R57	U14
LED11	R65	T16
LED12	R67	V15
LED13	R70	V14
LED14	R72	V12
LED15	R74	V11

2) Dvoubitový široký multiplexer 4 na 1

a) Výpis architektury VHDL ze zdrojového souboru

```
architecture Behavioral of mux_2bit_4to1 is
begin

    f_o <= a_i when (sel_i = "00") else
           b_i when (sel_i = "01") else
           c_i when (sel_i = "10") else
           d_i;

    -- WRITE "GREATER" AND "EQUALS" ASSIGNMENTS HERE

end architecture Behavioral;
```

b) Výpis stimulačního procesu VHDL ze souboru testbench

```
p_stimulus : process
begin
    -- Report a note at the beginning of stimulus process
    report "Stimulus process started" severity note;

    -- First test values
    s_d <= "00"; s_c <= "00"; s_b <= "00"; s_a <= "00";
    s_sel <= "00"; wait for 10 ns;

    s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "00";
    s_sel <= "00"; wait for 10 ns;
```

```

s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "11";
s_sel <= "00"; wait for 10 ns;


s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "00";
s_sel <= "01"; wait for 10 ns;

s_d <= "10"; s_c <= "01"; s_b <= "11"; s_a <= "00";
s_sel <= "01"; wait for 10 ns;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

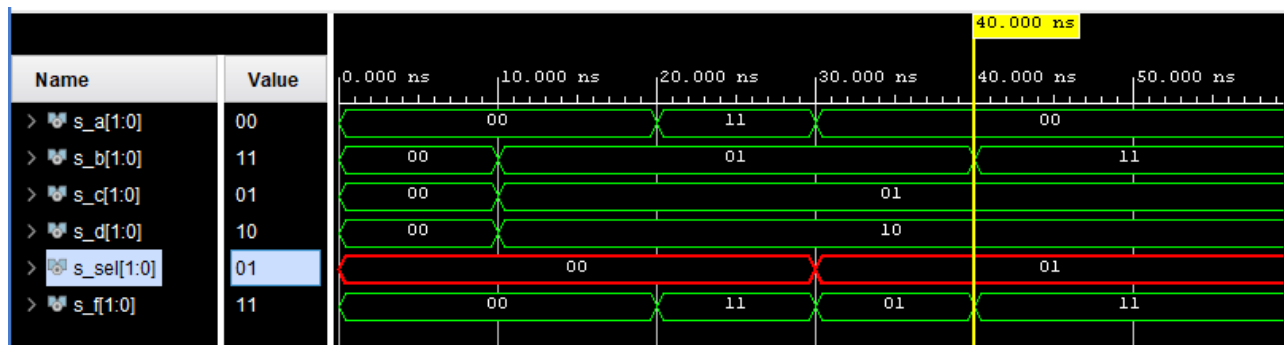c) Screenshot se simulovanými časovými průběhy



3) Výukový program Vivado (návod na základy Vivada)

(https://github.com/david3891/Digital-electronics-1/blob/main/Labs/03-vivado/n%C3%A1vod_vivado.pdf)